Pautes de correcció

Electrotecnia

SÈRIE 3

Primera part

Exercici 1

Q1 b

Q2 c **Q3** a

Q4 c

Q5 c

Exercici 2

a)
$$I = \frac{U_1}{R_1 + R_2} = \frac{20}{10 + 10} = 1$$
 A

b)
$$U(R_2) = R_2 I = 10$$
 V

c)
$$U(R_2) = U_2 = 10$$
 V

Alternativament

$$\begin{cases} U_1 = R_1 I + R_2 (I_2 + I) \\ U_2 = R_3 I_2 + R_2 (I_2 + I); \\ I_2 = 0 \end{cases} \begin{cases} 20 = 10I + 10 (I_2 + I) \\ U_2 = 5I_2 + 10 (I_2 + I) \Rightarrow \begin{cases} U_2 = 10 \text{ V} \\ I = 1 \text{ A} \\ I_2 = 0 \end{cases}$$

d)
$$P_1 = U_1 I = 20$$
 W; $P_2 = U_2 I_2 = 0$

OPCIÓ A

Exercici 3

a)
$$k = \frac{\Gamma}{I} = \frac{50}{40} = 1,25 \text{ V} \frac{\text{rad}}{\text{s}}$$

$$E = k\omega = 1,25.764 \frac{2\pi}{60} = 100 \text{ V}$$

b)
$$U = R_i I + E = 0.25 \cdot 40 + 100 = 110$$
 V

c)
$$\eta = 100 \frac{EI}{UI} = 100 \frac{100}{110} = 90,91 \%$$

Exercici 4

a)
$$X_L = \omega L = 2\pi f L = 100 \cdot \pi \cdot 0, 1 = 31,42 \Omega$$

$$Z = \sqrt{R^2 + X_1^2} = \sqrt{100^2 + 31,42^2} = 104,8$$
 Ω

Electrotecnia

$$I_{R} = \frac{U}{Z} = \frac{230}{104.8} = 2,194$$
 A

b)
$$Q = X_L I_R^2 = 31,42 \cdot 2,194^2 = 151,2 \text{ var}$$

c)
$$X_{\text{C}} = \frac{U^2}{Q} = \frac{230^2}{151,2} = 349,9 \quad \Omega \; ; \qquad C = \frac{1}{\omega X_{\text{C}}} = \frac{1}{100 \cdot \pi \cdot 349,9} = 9,097 \quad \mu\text{F}$$

OPCIÓ B

Exercici 3

a)
$$Z = \sqrt{R^2 + X^2} = \sqrt{2^2 + 0.4^2} = 2,040 \Omega$$
; $I = \frac{U}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 65,11 A$

b)
$$P = 3RI^2 = 3 \cdot 2 \cdot 65,11^2 = 25,43$$
 kW

c)
$$Q = 3XI^2 = 3 \cdot 0.4 \cdot 65.11^2 = 5.087$$
 kvar

d)
$$fdp = \cos \varphi = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{25,43}{\sqrt{25,43^2 + 5,087^2}} = 0,9806$$

Exercici 4

a)
$$I = \frac{P}{U} = \frac{200}{230} = 0,8696$$
 A

b)
$$\Delta U_{\text{max}} = 0.03 \cdot U = 6.9 \text{ V}$$

$$\Delta U_{\text{m\`ax}} = 2R_{\text{m\`ax}}I \Rightarrow R_{\text{m\`ax}} = \frac{\Delta U_{\text{m\`ax}}}{2I} = \frac{6.9}{2 \cdot 0.8696} = 3.967 \ \Omega$$

$$L_{\text{max}} = R_{\text{max}} \frac{S}{\rho} = 3,967 \frac{1,5}{0,01786} = 333,2 \text{ m}$$

c)
$$I_{CC} = \frac{U}{2R_{max}} = \frac{230}{2 \cdot 3,967} = 28,99 \text{ A}$$