Sèrie 2

Primera part

Exercici 1

Q1 c Q2 a Q3 a Q4 c Q5 a

Exercici 2

a)
$$I_2 = \frac{U_2 - V_3}{R_2} = 10 \text{ A}$$

b)
$$I_1 = \frac{U_1 - V_3}{R_1} = 10 \text{ A}$$

c)
$$R_3 = \frac{V_3}{I_1 + I_2} = 2\Omega$$

Segona part

OPCIÓ A

Exercici 3

a)
$$I_{R} = \frac{U}{R} = 29,23 \text{ A}$$
; $I_{X} = \frac{U}{X} = 12,67 \text{ A}$; $I_{AB} = \sqrt{I_{R}^{2} + I_{X}^{2}} = 31,86 \text{ A}$

b)
$$I_A = I_{AB}\sqrt{3} = 55,18 \text{ A}$$

c)
$$P = 3\frac{U^2}{R} = 33,32 \text{ kW}$$
; $Q = 3\frac{U^2}{X} = 14,44 \text{ kVAr}$; $S = \sqrt{P^2 + Q^2} = 36,32 \text{ kVA}$

Exercici 4

a)
$$\Re = \frac{e}{\mu_0 S} = 4,775 \text{ MA / Wb}$$

b)
$$\Phi_{\text{max}} = \frac{N\sqrt{2}I_{\text{ef}}}{\Re} = 0.1481 \text{ mWb}; \ B_{\text{max}} = \frac{\Phi_{\text{max}}}{S} = 0.2962 \text{ T}$$

OPCIÓ B

Exercici 3

a)
$$C_{12} = C_1 + C_2 = 20 \mu F$$

b)
$$\frac{1}{C_{eq}} = \frac{1}{C_{12}} + \frac{1}{C_3} \Rightarrow C_{eq} = 10 \,\mu\text{F}$$

c)
$$I = 0 A$$

d)
$$E = \frac{1}{2}C_{eq}U^2 = 12.5 \text{ mJ}$$

e)
$$\tau = RC_{eq} = 0.1 \text{ ms}$$

Exercici 4

a)
$$I = 10 \text{ A}$$

b)
$$p = 2$$

c)
$$S = \sqrt{3}UI = 6,582 \text{ kVA}$$
; $P_e = S \cos \varphi = 5,397 \text{ kW}$

d)
$$\eta = \frac{P}{P_e} = 0.9264$$
; $\eta(\%) = 92.64\%$

e)
$$\omega_{\text{nom}} = 1450 \frac{2\pi}{60} = 151.8 \text{ rad}; \quad \Gamma = \frac{P}{\omega_{\text{nom}}} = 32.93 \text{ Nm}$$