Pautes de correcció

Electrotècnia

Sèrie 3

Exercici 1

Q1 c Q2 c Q3 a Q4 c Q5 d

Exercici 2

a)
$$I = \frac{U}{R_1 + R_2} = 3 \text{ A}$$

b)
$$I = \frac{U}{R + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}} = 4A$$

c)
$$V_2 = U - R_1 I = 20 \text{ V}$$

$$V_1 = V_2 \frac{R_4}{R_3 + R_4} = 10 \text{V}$$

OPCIÓ A

Exercici 3

a)
$$\eta = 100 \frac{P}{UI} = 90 \%$$

b)
$$n = 1000 \,\mathrm{min^{-1}} \Rightarrow \omega = 104,72 \,\frac{\mathrm{rad}}{\mathrm{s}}$$
; $T = \frac{P}{\omega} = 5,157 \,\mathrm{Nm}$

$$T = k I \Rightarrow k = 0.2063 \frac{\text{Nm}}{\text{A}}; U = RI + k \omega \Rightarrow R = 0.096 \Omega$$

c)
$$T' = T/2 \Rightarrow I' = \frac{I}{2} = 12,5 \text{A}$$
; $\omega' = \frac{U - RI'}{k} = 110,54 \frac{\text{rad}}{\text{s}}$ $n' = 1056 \text{ min}^{-1}$

Exercici 4

a)
$$fdp = 1 \Rightarrow \varphi = 0 \Rightarrow X_L = X_C \Rightarrow 2\pi f L = \frac{1}{2\pi C} \Rightarrow f = 339.3 \text{ Hz}$$

b)
$$P = \frac{U^2}{R} = 529 \,\text{W}$$

Pautes de correcció

Electrotècnia

c)
$$X_{C50} = \frac{1}{2\pi 50C} = 14,47 \,\Omega$$
; $X_L = 2\pi 50L = 0,314 \,\Omega$; $Z = \sqrt{R^2 + (X_L - X_C)^2} = 101 \,\Omega$;

$$I = \frac{U}{Z} = 2,277 \,\mathrm{A}$$
;

$$Q = (X_L - X_C)I^2 = -73.4 \text{ VAr}$$

OPCIÓ B

Exercici 3

a)
$$I = \frac{U/\sqrt{3}}{\sqrt{R^2 + X^2}} = 21,44 \,\text{A}$$

b)
$$P = 3RI^2 = 13790 \text{ W}$$

c)
$$Q = 3XI^2 = 5516 \text{VAr}$$

d)
$$S = \sqrt{3} U I = 14852 \text{ VA}$$
; $\cos \varphi = \frac{P}{S} = 0.9285$

Exercici 4

a)
$$I = \frac{P}{U} = 10 \,\text{A}$$
;

b)
$$\frac{5}{100}U = 2R_{\text{max}}I \Rightarrow R_{\text{max}} = 0.575\Omega$$
; $R_{\text{max}} = \rho \frac{L}{S_{\text{min}}} \Rightarrow S_{\text{min}} = 1.86 \, \text{mm}^2$

c) $2.5 \,\mathrm{mm}^2$

Pautes de correcció

Electrotècnia

Sèrie 1

Exercici 1

Q1 c Q2 a Q3 c Q4 a Q5 b

Exercici 2

a)
$$R_3 = \frac{V_3}{A_3} = 2\Omega$$

b)
$$U_2 = R_2(A_3 - A_1) + V_3 = 16 \text{ V}$$


c)
$$U_1 = R_1 A_1 + V_3 \Rightarrow R_1 = 1\Omega$$

OPCIÓ A

Exercici 3

a)
$$I_L = \frac{V_1}{X_L} = 9 \,\text{A}$$
; $I_C = \frac{V_1}{X_C} = 4.5 \,\text{A}$

b)
$$I_R = I_L - I_C = 4.5 \,\text{A}$$

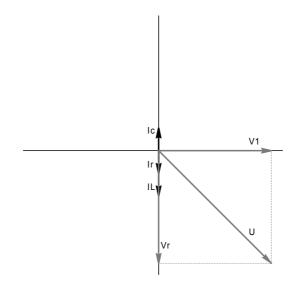

c)
$$U = \sqrt{V_r^2 + V_1^2} = \sqrt{(RI)^2 + V_1^2} = \sqrt{(40 \cdot 4.5)^2 + 180^2} = 254.6 \text{ V}$$

Pautes de correcció

Electrotècnia

Exercici 4

d)
$$\eta = 100 \frac{P}{\sqrt{3} UI \cos \varphi} = 90.56\%$$

e) 3 parells de pols

f)
$$n = 975 \,\text{min}^{-1} \Rightarrow \omega = 102,1 \,\frac{\text{rad}}{\text{s}}; T = \frac{P}{\omega} = 156,7 \,\text{Nm}$$

g) Estrella; $I_1 = 30 \,\mathrm{A}$

OPCIÓ B

Exercici 3

e)
$$Z = \sqrt{R^2 + X^2} = 10,77 \Omega$$
; $I_B = \frac{U}{Z} = 37,14 \text{ A}$

f)
$$I_L = \sqrt{3}I_B = 64,33 \,\text{A}$$

g)
$$P = 3RI_B^2 = 41381W$$

h)
$$Q = 3XI_B^2 = 16553 \text{VAr}$$

i)
$$S = \sqrt{3}UI = 44569 \text{ VA}; \cos \varphi = \frac{P}{S} = 0.928$$

Exercici 4

d)
$$P = UI \Rightarrow I = 17,39 \text{ A}$$

e)
$$R = \rho \frac{2l}{S} = 0.1339 \Omega$$
; $\Delta U(\%) = 100 \frac{RI}{U} = 1.01\%$

f) 20 A