Electrotècnia

SÈRIE 3

Primera part

Exercici 1

Q1 a

Q2 c

Q3 c

Q4 b

Q5 b

Exercici 2 a)
$$A_1 = \frac{U_1}{R_1} = \frac{100}{100} = 1 \text{ A}$$

b)
$$A_2 = \frac{U_1}{R_2} = \frac{100}{200} = 0.5 \text{ A}$$

c)
$$A_3 = 0 \text{ A}$$

d)
$$W_1 = U_1 \cdot I = U_1 \cdot (A_1 + A_2) = 100 \cdot (1 + 0.5) = 150 \text{ W}$$

OPCIÓ A

Exercici 3

a)
$$A_2 = \frac{V_2}{R_2} = \frac{200}{10} = 20 \text{ A}$$

b)
$$r_{\rm t} = \frac{U_{\rm 1N}}{U_{\rm 2N}} = \frac{400}{230} \rightarrow r_{\rm t} = \frac{A_2}{A_1} = \frac{400}{230} \rightarrow A_1 = \frac{A_2}{r_{\rm t}} = \frac{20 \cdot 230}{400} = 11.5 \text{ A}$$

c)
$$W_1 = R_1 A_1^2 + R_2 A_2^2 \rightarrow R_1 = \frac{W_1 - R_2 A_2^2}{A_1^2} = \frac{5300 - 10 \cdot 20^2}{11,5^2} = 9,83 \Omega$$

d)
$$U_1 = \frac{W_1}{A_1} = \frac{5300}{11.5} = 460.9 \text{ V}$$

Exercici 4

a)
$$\eta(\%) = 100 \frac{P}{UI} = 100 \frac{250}{36.7.62} = 91.13 \%$$

b)
$$E = \frac{P}{I} = \frac{250}{7.62} = 32.81 \text{ V}; \quad R_i = \frac{U - E}{I} = \frac{36 - 32.81}{7.62} = 0.419 \Omega$$

c)
$$E' = U - R_i \cdot 0.6 \cdot I = 36 - 0.419 \cdot 0.6 \cdot 7.62 = 34.08 \text{ V}$$

$$n' = n \frac{E'}{E} = 3850 \frac{34,08}{32,81} = 3999 \text{ min}^{-1}$$

PAU 2014

Pautes de correcció

Electrotècnia

OPCIÓ B

Exercici 3

a)
$$X_{\rm C} = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi 50 \cdot 20 \cdot 10^{-6}} = 159,2 \,\Omega$$

 $A_1 = \frac{U}{X_{\rm C}} = \frac{400}{159,2} = 2,51 \,\text{A}$

b)
$$A_2 = \frac{U}{R} = \frac{400}{100} = 4 \text{ A}$$

c)
$$A_3 = \sqrt{A_1^2 + A_2^2} = \sqrt{2,51^2 + 4^2} = 4,72 \text{ A}$$

d)
$$A_4 = \sqrt{3}A_3 = \sqrt{3} \cdot 4,72 = 8,18 \text{ A}$$

e)
$$P_{\text{Total}} = 3 \cdot R \cdot A_2^2 = 3 \cdot 100 \cdot 4^2 = 4800 \text{ W}$$

Exercici 4

a)
$$f = \frac{1}{T} = \frac{1}{4 \cdot 1 \cdot 10^{-3}} = 250 \text{ Hz}$$

b)
$$U_{\text{max}} = \frac{R_1 + R_2}{R_2} U_{\text{R2 max}} = \frac{10 + 30}{30} \cdot 3.4 \cdot 20 = 90.67 \text{ V}$$

c)
$$U_{\text{RMS}} = \frac{U_{\text{max}}}{\sqrt{2}} = \frac{90,67}{\sqrt{2}} = 64,11 \text{ V}$$

PAU 2014

Pautes de correcció

Electrotècnia

SÈRIE 4

Primera part

Exercici 1

Q1 a **Q2** a **Q3** a **Q4** d **Q5** d

Exercici 2

a)

$$\begin{cases} R_{1}I_{1} + R_{2}(I_{1} + I_{2}) = U_{1} + U_{2} + U_{3} \\ R_{3}I_{2} + R_{2}(I_{1} + I_{2}) = U_{4} \end{cases} \rightarrow \begin{cases} (R_{1} + R_{2})I_{1} + R_{2}I_{2} = U_{1} + U_{2} + U_{3} \\ R_{2}I_{1} + (R_{2} + R_{3})I_{2} = U_{4} \end{cases}$$

$$\begin{bmatrix} R_{1} + R_{2} & R_{2} \\ R_{2} & R_{2} + R_{3} \end{bmatrix} \begin{bmatrix} I_{1} \\ I_{2} \end{bmatrix} = \begin{bmatrix} U_{1} + U_{2} + U_{3} \\ U_{4} \end{bmatrix} \rightarrow \begin{bmatrix} 13 & 10 \\ 10 & 15 \end{bmatrix} \begin{bmatrix} I_{1} \\ I_{2} \end{bmatrix} = \begin{bmatrix} 22 \\ 10 \end{bmatrix}$$

$$I_1 = 2,421 \text{ A}$$

 $I_2 = -0,947 \text{ A}$

b)
$$P_{R2} = R_2(I_1 + I_2)^2 = 10(2,421 - 0,947)^2 = 21,73 \text{ W}$$

c)

$$\begin{split} P_{\text{U1}} &= U_1 I_1 = 5 \cdot 2,421 = 12,105 \text{ W} \\ P_{\text{U2}} &= U_2 I_1 = 7 \cdot 2,421 = 16,947 \text{ W} \\ P_{\text{U3}} &= U_3 I_1 = 10 \cdot 2,421 = 24,21 \text{ W} \\ P_{\text{U4}} &= U_4 I_2 = 10 \cdot (-0,947) = -9,47 \text{ W} \end{split}$$

OPCIÓ A

Exercici 3

a)
$$p = 4$$

b)
$$\Gamma = \frac{P}{\omega} = \frac{4000}{728 \frac{2\pi}{60}} = 52,47 \text{ N m}$$

c)
$$\eta(\%) = 100 \frac{P}{\sqrt{3}UI\cos\varphi} = 100 \frac{4000}{\sqrt{3} \cdot 400 \cdot 10, 2 \cdot 0, 67} = 84,48 \%$$

d) 4 kW

PAU 2014

Pautes de correcció

Electrotècnia

Exercici 4

b)
$$I = \frac{P}{U} = \frac{12}{15} = 0.8 \text{ A}$$

$$230 = RI + 12 \cdot U$$
 \rightarrow $R = \frac{230 - 12 \cdot U}{I} = \frac{230 - 12 \cdot 15}{0.8} = 62,5 \Omega$

b)
$$P_{\rm R} = RI^2 = 62.5 \cdot 0.8^2 = 40 \,\text{W}$$

c)
$$P_{\text{Total}} = P_{\text{R}} + 12 \cdot P_{\text{Làmpada}} = 40 + 12 \cdot 12 = 184 \text{ W}$$

d)
$$P = 0 \text{ W}$$

OPCIÓ B

Exercici 3

a)
$$V_2 = R_2 A_2 = 50 \cdot 1,437 = 71,85 \text{ V}$$

b)
$$A_3 = \frac{V_2}{X_L - X_C} = \frac{71,85}{50 - 30} = 3,593 \text{ A}$$

c)
$$A_1 = \sqrt{A_2^2 + A_3^2} = \sqrt{1,437^2 + 3,593^2} = 3,87 \text{ A}$$

d)
$$W_2 = R_2 A_2^2 = 50 \cdot 1,437^2 = 103,25 \text{ W}$$

e)
$$W_1 = R_1 A_1^2 + W_2 = 50 \cdot 3,87^2 + 103,25 = 852,1 \text{ W}$$

Exercici 4

a)
$$\eta(\%) = 100 \frac{P}{U \cdot I} = 100 \frac{60}{36 \cdot 2} = 83,33 \%$$

b)
$$\Gamma = \frac{P}{\omega} = \frac{60}{7840 \frac{2\pi}{60}} = 73,08 \text{ mN m}$$

c)
$$E = \frac{P}{I} = \frac{60}{2} = 30 \text{ V}$$

$$R_{\rm i} = \frac{U - U_{\rm b} - E}{I} = \frac{36 - 1,2 - 30}{2} = 2,4 \ \Omega$$

d)
$$E' = U' - R_i \cdot 0.7 \cdot I - U_b = 30 - 2.4 \cdot 0.7 \cdot 2 - 1.2 = 25.44 \text{ V}$$

$$n' = n \frac{E'}{F} = 7840 \frac{25,44}{30} = 6648,3 \text{ min}^{-1}$$