PAU 2015

Criteris de correcció

Electrotecnia

SÈRIE 5

Primera part

Exercici 1

Q1 d

Q2 a **Q3** c **Q4** d **Q5** c

Exercici 2

a)
$$I_1 = \frac{P_{U_1}}{U_1} = \frac{60}{24} = 2,5 \text{ A}$$

b)
$$\begin{cases} R_1 I_1 + R_3 (I_1 - I_2) = U_1 \\ R_3 (I_1 - I_2) - R_2 I_2 = U_2 \end{cases} \rightarrow \begin{cases} 5 \cdot 2.5 + R_3 (2.5 - I_2) = 24 \\ R_3 (2.5 - I_2) - 7 I_2 = 10.1 \end{cases} \rightarrow \begin{cases} 2.5 R_3 - R_3 I_2 = 11.5 \\ 2.5 R_3 - R_3 I_2 - 7 I_2 = 10.1 \end{cases} \rightarrow \begin{cases} I_2 = \frac{2.5 R_3 - 11.5}{R_3} \\ 2.5 R_3 - R_3 \frac{2.5 R_3 - 11.5}{R_3} - 7 \frac{2.5 R_3 - 11.5}{R_3} = 10.1 \end{cases}$$

$$\begin{cases} I_2 = \frac{2.5 R_3 - 11.5}{R_3} \\ 11.5 - 7 \frac{2.5 R_3 - 11.5}{R_3} = 10.1 \end{cases} \rightarrow \begin{cases} I_2 = \frac{2.5 R_3 - 11.5}{R_3} \\ \frac{2.5 R_3 - 11.5}{R_3} = 0.2 \end{cases} \rightarrow \begin{cases} I_2 = 0.2 A \\ R_3 = 5 \Omega \end{cases}$$

OPCIÓ A

a)
$$A_1 = \frac{U}{\sqrt{R^2 + X_L^2}} = \frac{400}{\sqrt{50^2 + 100^2}} = 3,578 \text{ A}$$

b)
$$A_2 = \sqrt{3} A_1 = \sqrt{3} \cdot 3,578 = 6,197 A$$

c)
$$V_1 = R A_1 = 50 \cdot 3,578 = 178,9 \text{ V}$$

d)
$$V_2 = X_L A_1 = 100 \cdot 3,578 = 357,8 \text{ V}$$

e)
$$P = 3 R A_1^2 = 3 \cdot 50 \cdot 3,578^2 = 1920 W$$

Exercici 4

a) Escala de tensió =
$$\frac{U_{\text{G1 màx}}}{\text{Núm.Div}} = \frac{36}{3.6} = 10 \frac{\text{V}}{\text{div}}$$

b)
$$f = \frac{1}{T} = \frac{1}{6 \text{ div } \cdot 2 \frac{\mu s}{\text{div}}} = 83,33 \text{ kHz}$$

c) Semiperiode positiu:
$$P_{\rm p} = \frac{U_{\rm G1}^2}{R_{\rm Eq}} = \frac{U_{\rm G1}^2}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{36^2}{10 + \frac{10 \cdot 10}{10 + 10}} = 86,4 \text{ W}$$

Semiperiode negatiu:
$$P_n = 0 \text{ W}$$

Semiperiode negatiu:
$$P_n = 0 \text{ W}$$

Potència mitja: $P = \frac{P_p + P_n}{2} = \frac{86,4+0}{2} = 43,2 \text{ W}$

Criteris de correcció

Electrotecnia

OPCIÓ B

Exercici 3

a)
$$\eta(\%) = 100 \frac{P_{\text{N}}}{P} = 100 \frac{110000}{\sqrt{3} \cdot 690 \cdot 120 \cdot 0.84} = 91.31 \%$$

Alternativament,
$$\eta(\%) = 100 \; \frac{P_{\rm N}}{P} = 100 \; \frac{110000}{\sqrt{3} \cdot 400 \cdot 208 \cdot 0,84} = 90,87 \; \%$$
 b)
$$\Gamma = \frac{P_{\rm N}}{\omega_{\rm N}} = \frac{110000}{1450 \frac{2 \, \pi}{60}} = 724,4 \; {\rm N \; m}$$

b)
$$\Gamma = \frac{P_{\text{N}}}{\omega_{\text{N}}} = \frac{110000}{1450\frac{2\pi}{60}} = 724.4 \text{ N m}$$

c)
$$Q=\sqrt{3}~U_{\rm N}~I_{\rm N}\sin\varphi_{\rm N}=\sqrt{3}\cdot690\cdot120\cdot\sqrt{1-0.84^2}=77.81$$
 kvar Alternativament,

$$Q = \sqrt{3} U_{\text{N}} I_{\text{N}} \sin \varphi_{\text{N}} = \sqrt{3} \cdot 400 \cdot 208 \cdot \sqrt{1 - 0.84^2} = 78.19 \text{ kvar}$$

- d) 400 V
- e) 208 A

Exercici 4

a)

$$\begin{cases} R_2 I_2 = R_3 I_3 \\ R_2 I_2^2 + R_3 I_3^2 = W \end{cases} \rightarrow \begin{cases} I_2 = \frac{R_3 I_3}{R_2} \\ R_2 \left(\frac{R_3 I_3}{R_2}\right)^2 + R_3 I_3^2 = W \end{cases} \rightarrow \begin{cases} I_2 = \frac{R_3 I_3}{R_2} \\ \frac{(R_3 I_3)^2}{R_2} + R_3 I_3^2 = W \end{cases}$$

$$\begin{cases} I_2 = \frac{2 \cdot I_3}{3} \\ \frac{(2 \cdot I_3)^2}{3} + 2 I_3^2 = 187.5 \end{cases} \rightarrow \begin{cases} I_2 = \frac{2 \cdot I_3}{3} = \frac{2 \cdot 7.5}{3} = 5 \text{ A} \\ I_3 = \sqrt{\frac{187.5 \cdot 3}{10}} = 7.5 \text{ A} \end{cases}$$

Alternativament:
$$R_{\rm Eq.2,3} = \frac{R_2\,R_3}{R_2 + R_3} = \frac{3\cdot 2}{3+2} = 1,2\,\Omega \qquad \qquad U_{\rm Eq.2,3} = \sqrt{W\,R_{\rm Eq.2,3}} = \sqrt{187,5\cdot 1,2} = 15\,V$$

$$I_2 = \frac{U_{\rm Eq.2,3}}{R_2} = \frac{15}{3} = 5\,A \qquad \qquad I_3 = \frac{U_{\rm Eq.2,3}}{R_3} = \frac{15}{2} = 7,5\,A$$
 b)
$$A_1 = I_2 + I_3 = 5 + 7,5 = 12,5\,A$$
 c)

b)
$$A_1 = I_2 + I_3 = 5 + 7.5 = 12.5 \text{ A}$$

$$Z = \frac{U}{A_1} = \frac{100}{12.5} = 8 \Omega$$

$$Z = \sqrt{\left(R_1 + R_{\text{Eq.2,3}}\right)^2 + X_L^2}$$

$$X_L = \sqrt{Z^2 - \left(R_1 + R_{\text{Eq.2,3}}\right)^2} = \sqrt{8^2 - (5 + 1.2)^2} = 5.056 \Omega$$

$$L = \frac{X_L}{2 \pi f} = \frac{5.06}{2 \pi 50} = 16.09 \text{ mH}$$